

EXPERIMENT-03

AIM:

To simulate and synthesis multiplier using Xilinx ISE.

APPARATUS REQUIRED: Xilinx 14.7 Spartan6 FPGA

PROCEDURE:

STEP:1 Start the Xilinx navigator, Select and Name the New project.

STEP:2 Select the device family, device, package and speed.

STEP:3 Select new source in the New Project and select Verilog Module as the Source type.

STEP:4 Type the File Name and Click Next and then finish button. Type the code and save it.

STEP:5 Select the Behavioral Simulation in the Source Window and click the check syntax.

STEP:6 Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

STEP:7 Select the Implementation in the Sources Window and select the required file in the Processes Window.

STEP:8 Select Check Syntax from the Synthesize XST Process. Double Click in the FloorplanArea/IO/Logic-Post Synthesis process in the User Constraints process group. UCF(User constraint File) is obtained.

STEP:9 In the Design Object List Window, enter the pin location for each pin in the Loc column Select save from the File menu.



STEP:10 Double click on the Implement Design and double click on the Generate Programming File to create a bitstream of the design.(.v) file is converted into .bit file here.

STEP:11 On the board, by giving required input, the LEDs starts to glow light, indicating the output.

Logic Diagram

2 bit Multiplier:

of decimal numbers

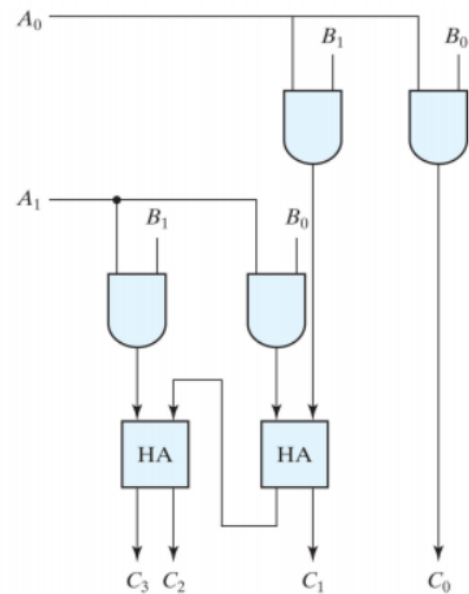 

VERILOG CODE:

```
module ha(a,b,sum,carry);
```

```
input a,b;
```

```
output sum,carry ;
```

```
xor x1(sum,a,b);
```

```
and a1(carry,a,b);
```

```
endmodule
```

```
module mul_2(a,b,c);
```

```
input[1:0]a,b;
```

```
output[3:0]c;
```

```
wire w1,w2,w3,w4;
```

```
and g1(c[0],a[0],b[0]);
```

```
and g2(w1,a[0],b[1]);
```

```
and g3(w2,a[1],b[0]);
```

```

and g4(w3,a[1],b[1]);


ha ha1(w1,w2,c[1],w4);

ha ha2(w3,w4,c[2],c[3]);


endmodule

```

OUTPUT:

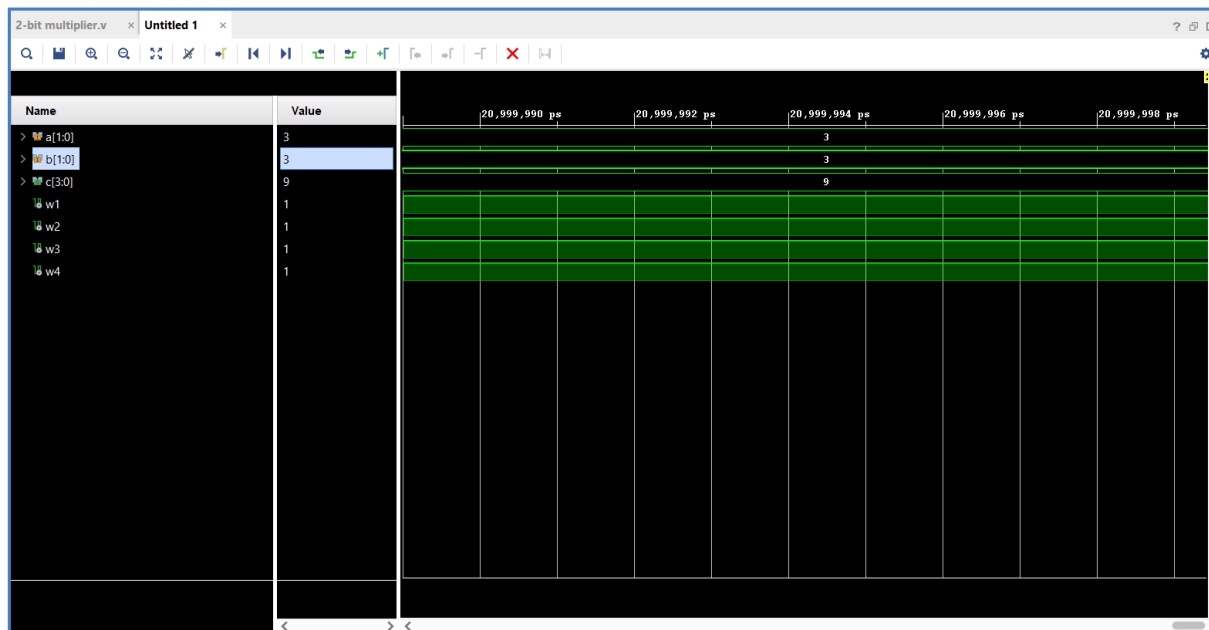

4 bit Multiplier:

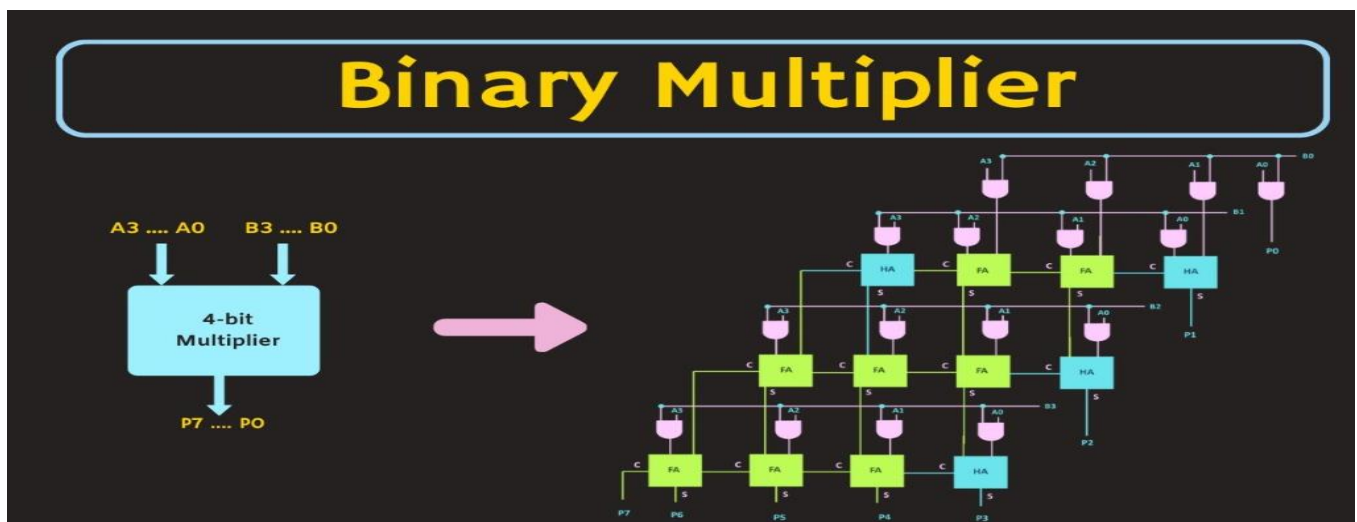

VERILOG CODE:

```
module ha(a,b,e,c);  
input a,b;  
output e,c;  
xor (e,a,b);  
and (c,a,b);  
endmodule
```

```
module fa(a,b,c,sum,carry);  
input a,b,c;  
output sum,carry;  
wire w1,w2,w3;  
xor g1(w1,a,b);  
xor g2(sum,w1,c);  
and g3(w2,a,b);  
and g4(w3,w1,c);  
or g5(carry,w3,w2);  
endmodule
```


```
module mul(x,y,z);  
input [3:0]x,y;  
output [7:0]z;  
wire [17:1]w;  
and (z[0],x[0],y[0]);  
ha ha1(x[1]&y[0],x[0]&y[1],z[1],w[1]);  
fa fa1(x[2]&y[0],x[1]&y[1],w[1],w[5],w[2]);
```

```

fa fa2(x[3]&y[0],x[2]&y[1],w[2],w[6],w[3]);
ha ha2(x[3]&y[1],w[3],w[7],w[4]);
ha ha3(w[5],x[0]&y[2],z[2],w[8]);
fa fa3(w[6],x[1]&y[2],w[8],w[12],w[9]);
fa fa4(w[7],x[2]&y[2],w[9],w[13],w[10]);
fa fa5(w[4],x[3]&y[2],w[10],w[14],w[11]);
ha ha4(w[12],x[0]&y[3],z[3],w[15]);
fa fa6(w[13],x[1]&y[3],w[15],z[4],w[16]);
fa fa7(w[14],x[2]&y[3],w[16],z[5],w[17]);
fa fa8(w[11],x[3]&y[3],w[17],z[6],z[7]);
endmodule

```

OUTPUT:

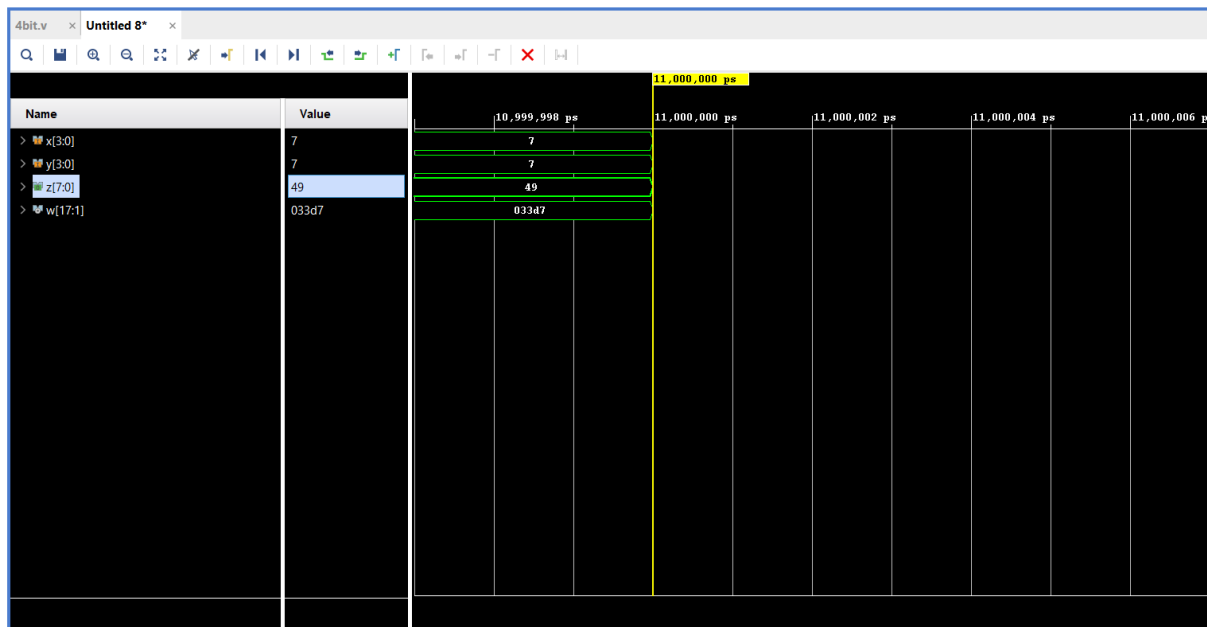

RESULT:

Thus , the given 2bit multiplier and 4 bit multiplier are simulated and synthesis are executed successfully.

